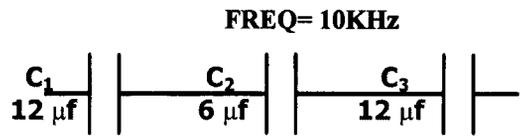


34. Calculate: (FIG 11)

- a. C_T :
- b. X_{CT}


FIG 11



35. Calculate: (FIG 12)

- a. C_{EQ} :
- b. X_{CEQ} :


FIG 12

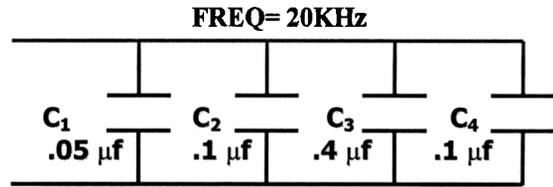

36. Calculate: (FIG 12)

- a. C_{EQ} : _____
- b. C_T : _____
- c. X_{CEQ} : ____
- d. X_{CT} : _____
- e. Z : _____
- f. E_{CEQ} : _____

FIG 12

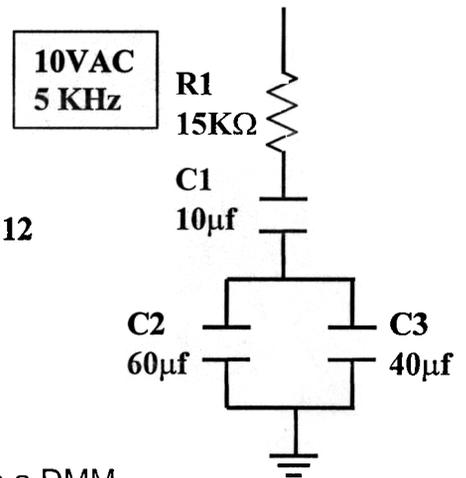


37. T or F You can measure capacitive reactance with a DMM.

38. What happens to capacitive reactance when frequency increases?

39. Calculate: (FIG 13)

- a. X_{L1} :
- b. X_{C1} : _____
- c. Z : _____

FIG 13

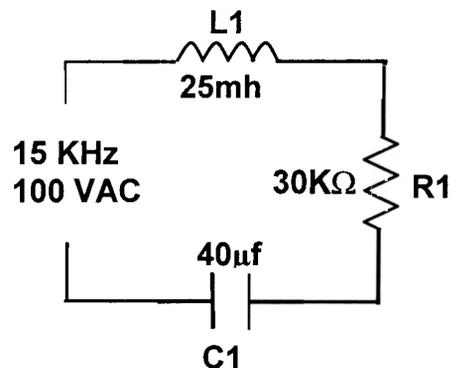

40. What is the formula for impedance in an LCR circuit?

41. What is the phase relation between E_C and E_L ?